

## Measurement Methods in Physics I

Fall 2016


### Exercise 3

27.9. - 29.9.

**Hand-in assignments. You have to return an answer sheet, even if it would be empty.**

Return by 22.9.2016 16:00.

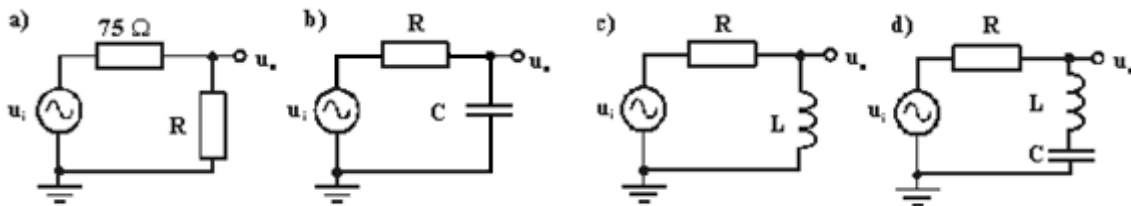1. Calculate the amplitudes and phases of the output signals  $u_o$  when  $f = 10 \text{ kHz}$ ,  $u_i = 12 \text{ V} \cdot \sin(2\pi \cdot f \cdot t)$ ,  $R = 180\Omega$ ,  $C = 470 \text{ nF}$ , ja  $L = 680 \mu\text{H}$ . *Hint: Voltage division can also be calculated for reactive components.*



2. Examine the circuits from 1 as filters. Make Bode-plots of the amplitude response for each circuit and determine the passband, stopband, -3dB cutoff frequency and slope of the stopband (decibels per decade) for each. The Bode-plot can be made using e.g. Matlab or LTspice.

3. a) How big can the rms-value of the noise be if a voltage signal, which fluctuates between 10 mV and 100 mV, is measured, is measured and the desired SNR is 25dB?

b) You are transmitting a voltage signal, which fluctuates between 0 V and 10 V, from one device to another. The analog transmission and reception adds a noise to the signal with an rms-value of 25 mV. You can avoid the noise by transferring the signal digitally. You have an A/D-converter at your disposal with a resolution of 8 bits and according to the data sheet the conversion precision is  $2 \times \text{LSB}$ . Does the use of the A/D-converter reduce the uncertainty of the signal?

**"Check box"-assignments. Bring these to the exercise session.**

4. a) What does crosstalk in a measurement device mean?

b) What causes Johnson noise and how can you reduce it? Calculate the Johnson noise in a  $10 \text{ k}\Omega$  resistor, when the frequency band is  $1 \text{ kHz} - 1 \text{ MHz}$  and the temperature is  $20 \text{ }^\circ\text{C}$ .

c) The mutual capacitance between the channels of a signal generator is  $100 \text{ pF}$ . How large is the capacitive coupling into channel 1 if a voltage signal passes through channel 2 with rms-value  $U=500 \text{ mV}$  and frequency  $1 \text{ kHz}$ . A load  $R_L = 1 \text{ k}\Omega$  is connected to channel 1.

5. a) Explain what the so called four-terminal sensing is.

b) Why is four-terminal sensing better than two-terminal sensing?