
 


# Electronics II – Chapter 4


## Boolean Algebra and Logic Simplification

 


**FIGURE 4-3** Application of commutative law of addition.




**FIGURE 4-4** Application of commutative law of multiplication.

 


**FIGURE 4-5** Application of associative law of addition.

 

**FIGURE 4-6** Application of associative law of multiplication.

 

**FIGURE 4-7** Application of distributive law.

 

**TABLE 4-1**

## Basic rules of Boolean algebra.

---

**1.**  $A + 0 = A$

**2.**  $A + 1 = 1$

**3.**  $A \cdot 0 = 0$

**4.**  $A \cdot 1 = A$

**5.**  $A + A = A$

**6.**  $A + \bar{A} = 1$

**7.**  $A \cdot A = A$

**8.**  $A \cdot \bar{A} = 0$

**9.**  $\bar{\bar{A}} = A$

**10.**  $A + AB = A$


**11.**  $A + \bar{A}B = A + B$

**12.**  $(A + B)(A + C) = A + BC$ 

---


$A$ ,  $B$ , or  $C$  can represent a single variable or a combination of variables.

**FIGURE 4-8**

 





**FIGURE 4-9**

 

**FIGURE 4-10**

 

**FIGURE 4-11**

 


**FIGURE 4-12**




$$X = A + A = A$$

**FIGURE 4-13**

 


**FIGURE 4-14**

  


$$X = A \cdot A = A$$

**FIGURE 4-15**



**FIGURE 4-16**

 

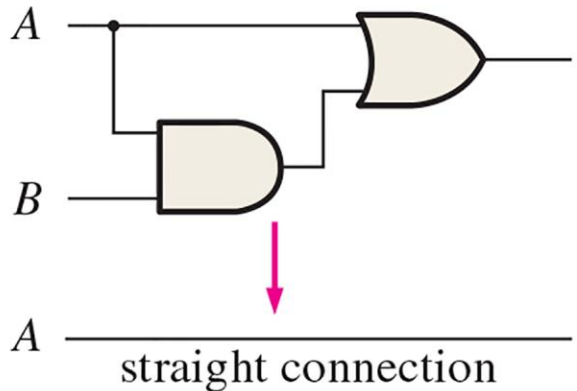


**TABLE 4-2**

Rule 10:  $A + AB = A$ . Open file T04-02 to verify.

$A$	$B$	$AB$	$A + AB$
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

↑ equal ↑

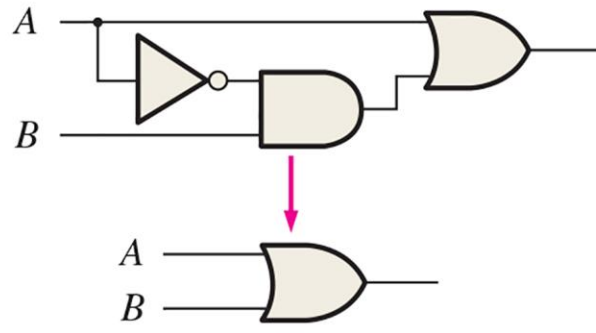


**TABLE 4-3**

Rule 11:  $A + \bar{A}B = A + B$ . Open file T04-03 to verify.

$A$	$B$	$\bar{A}B$	$A + \bar{A}B$	$A + B$
0	0	0	0	0
0	1	1	1	1
1	0	0	1	1
1	1	0	1	1

↑ equal ↑




**TABLE 4-4**

Rule 12:  $(A + B)(A + C) = A + BC$ . Open file T04-04 to verify.


$A$	$B$	$C$	$A + B$	$A + C$	$(A + B)(A + C)$	$BC$	$A + BC$
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

↑ equal ↑

**FIGURE 4-17** Gate equivalencies and the corresponding truth tables that illustrate DeMorgan's theorems. Notice the equality of the two output columns in each table. This shows that the equivalent gates perform the same logic function.

 


Inputs		Output	
$X$	$Y$	$\overline{XY}$	$\overline{X} + \overline{Y}$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

 

Inputs		Output	
$X$	$Y$	$\overline{X + Y}$	$\overline{\overline{X} \overline{Y}}$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

**FIGURE 4-18** A combinational logic circuit showing the development of the Boolean expression for the output.

 


**TABLE 4–5**


Truth table for the logic circuit in Figure 4–18.

Inputs				Output
<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	$A(B + CD)$
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

**FIGURE 4-20** Gate circuits for Example 4-9.

 


**FIGURE 4-22** Implementation of the SOP (Sum-Of-Products) expression  $AB + BCD + AC$ .

 




**FIGURE 4-23** This NAND/NAND implementation is equivalent to the AND/OR in Figure 4-22.

 


**FIGURE 4-24** Implementation of the POS (Sum-Of-Products) expression  $(A + B)(B + C + D)(A + C)$ .

 

**FIGURE 4-49** Illustration of the three levels of abstraction for describing a logic function.

**Highest level:** The truth table or state diagram

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>X</i>
0	0	0	0	0
0	0	0	1	0
⋮	⋮	⋮	⋮	⋮
1	1	1	1	1

 


**Middle level:** The Boolean expression, which can be derived from a truth table or schematic


$$X = AB + CD$$

Logic function


**Lowest level:** The logic diagram (schematic)

 

**FIGURE 4-50** Seven-segment display.

 

(a) Segment arrangement

 


(b) Formation of the ten digits and certain letters

**TABLE 4-14**

Active segments for each of the five letters used in the system display.

Letter	Segments Activated
A	<i>a, b, c, e, f, g</i>
b	<i>c, d, e, f, g</i>
C	<i>a, d, e, f</i>
d	<i>b, c, d, e, g</i>
E	<i>a, d, e, f, g</i>

**FIGURE 4-51** Hexadecimal-to-7-segment decoder for letters *A* through *E*, used in the system.

 


(a)


Letter	Hexadecimal Inputs				Segment Outputs						
	$H_3$	$H_2$	$H_1$	$H_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
A	1	0	1	0	0	0	0	1	0	0	0
b	1	0	1	1	1	1	0	0	0	0	0
C	1	1	0	0	0	1	1	0	0	0	1
d	1	1	0	1	1	0	0	0	0	1	0
E	1	1	1	0	0	1	1	0	0	0	0
F	1	1	1	1	0	1	1	1	0	0	0

(b)


**FIGURE 4-52** Minimization of the expressions for segments *a*, *b*, and *c*.

 

(a)

 


(b)

 

(c)

**FIGURE 4-53** Segment-*b* and segment-*c* logic circuits.

 



**FIGURE 4-54** Multisim circuit screen for decoder and display.

